

Data and Calculations relating to the 'Ringwood Energy Recycler' Experiment

1) Measure times to discharge Battery voltage from 4.2V to 3.45V

(The following times are averaged from several tests; representative graphs are shown in Fig. 3 - Fig. 6)

NIMH + 268R:

42.5h

NIMH + LED cluster + 78R:

45h

NO FB ('No Feedback') cct:

30.5h

WITH FB ('With Feedback') cct:

60.5h

2) Derive Vav from resistor/led cluster discharge results

For Vav = 3.86V;

(discharge current using 268R)

Idis:

$$3.86V / 268R = 14.4mA$$

(discharge current using 78R, LED cluster @ 2.8V forward voltage)

Iled:

$$(3.86V - 2.8V) / 78R = 13.59mA$$

(confirm Iled by comparing discharge times)

Iled:

$$14.4mA * 42.5h / 45h = 13.6mA$$

3) Derive Currents

NIMH + R

Idis:

$$3.86V / 268R = 14.4mA$$

(The following current paths are identified in Fig. 1)

NO FB

Iin:

$$14.4mA * 42.5h / 30.5h = 20.1mA$$

WITH FB

Ivirtual:

$$14.4mA * 42.5h / 60.5h = 10.1mA$$

Ifb:

$$20.1mA - 10.1mA = 10mA$$

4) Calculate Energy and Work totals & Efficiencies

(a factor of 3.6 is used to convert mWh to Joules)

NIMH + R

Etot: (total energy drawn from battery by 268R resistor)
 $3.86V \times 14.4mA \times 42.5h \times 3.6 = 8504J$

NO FB

Etot: (total energy drawn from battery by circuit)
 $3.86V \times 20.3mA \times 30.5h \times 3.6 = 8603J$

Eled: (work done by LEDs)

$$2.8V \times 10.1mA \times 30.5h \times 3.6 = 3105J$$

Enimh: (work done recharging spare NiMH)

$$3.86V \times 10mA \times 30.5h \times 3.6 = 4238J$$

7343J (quantifiable-work done)

quantifiable-work efficiency (NO FB)

$$n1 = 7343J / 8603J = 0.85$$

(quantifiable-work done / total energy input to cct)

(the mid-duration LED output was measured as approx. 147 foot-candles at 6")

WITH FB

Etot: (total energy drawn from battery by circuit)
 $3.86V \times 20.1mA \times 60.5h \times 3.6 = 16898J$

Eled: (work done by LED cluster)

$$2.8V \times 10.1mA \times 60.5h \times 3.6 = 6159J$$

Enimh: (work done recharging supply NiMH)

$$3.86V \times 10mA \times 60.5h \times 3.6 = 8407J$$

14566J (quantifiable-work done)

quantifiable-work efficiency (WITH FB)

$$n2 = 14566J / 16898J = 0.86$$

(quantifiable-work done / total energy input to cct)

(the mid-duration LED output was measured as approx. 146 foot-candles at 6")

quantifiable-work efficiency (WITH FB)

$$n3 = 14566J / 8504J = 1.7$$

(total work done / total original energy supplied)

total system efficiency (WITH FB)

$$n4 = 16898J / 8504J = 1.99$$

(total energy converted / total original energy supplied)

5) Cross-check extended work values

The 'No-Feedback' cct converts 3105J in the LED cluster, and it stores 4238J in the spare NiMH, so the extra work done in the 'With-Feedback' cct must be due to the equivalent of this 4238J stored back in the battery

If we subtract the original supply value, 8504J, from the total input supply to the 'With-Feedback' cct, 16898J, we see that the equivalent of that 4238J energy stored (ie. as recharged previously into the spare NiMH) has now enabled:

8394J of extra energy
to be supplied to the 'With-Feedback' cct, which results in (14566J - 7343J) = 7223J of extra quantifiable-work done

As a check, since the cct, on its own, is 86% work-efficient, that 7223J of extra work done would be equivalent to

$$(7233J / 0.86) = 8399J \text{ of extra energy input}$$

(See below for graphical data)

SRobson
27 May 2019

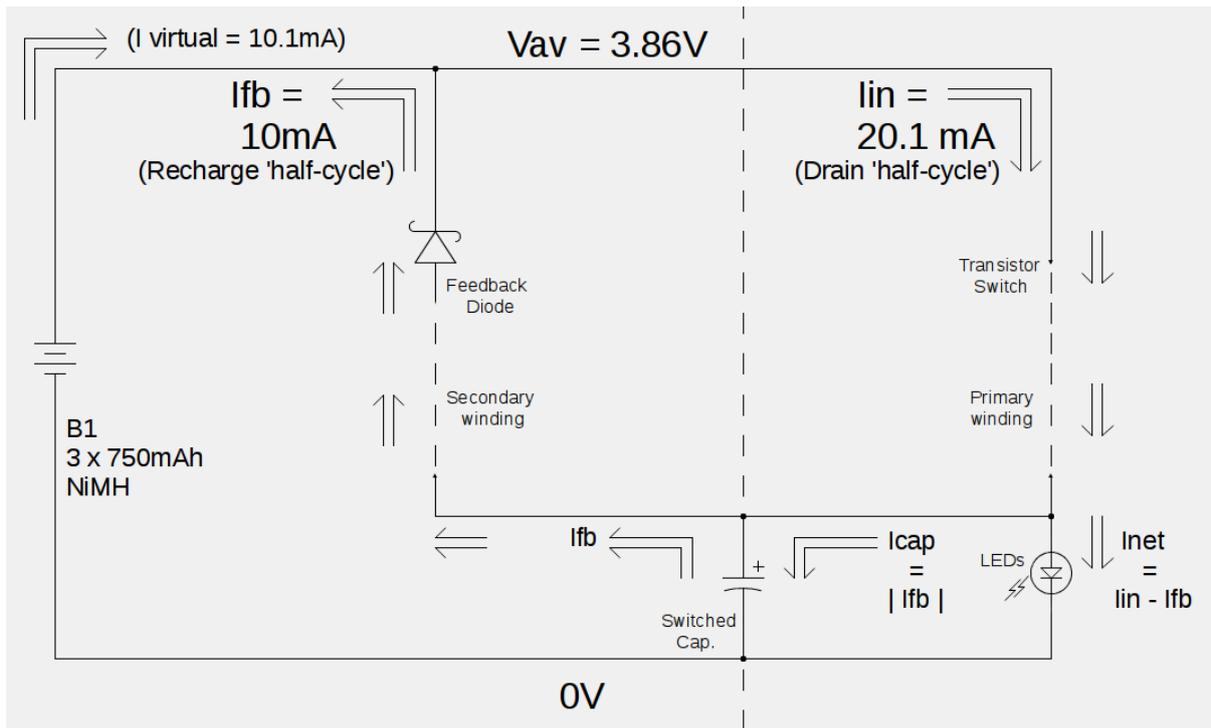


Fig 1 - Switched Current flows

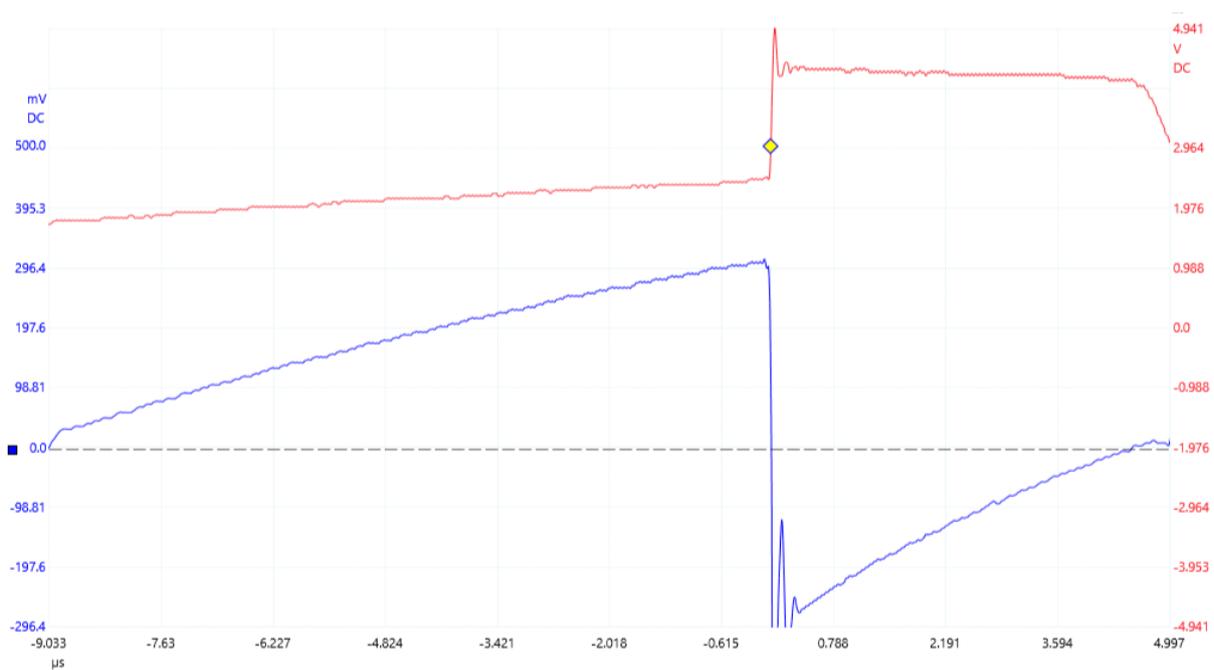


Fig 2 - Feedback pulse (Red),
Bi-polar current pulses (Blue)
(from/to supply battery for 'With Feedback' cct)

Two bi-polar current pulses occur within each cycle (approx. 14 μ s total duration); the positive-going 'sawtooth' pulse is the supply current (I_{in}), and the negative-going 'sawtooth' pulse is the feedback current to the battery (I_{fb}). (The bi-polar pulse trace was obtained just for illustrative purposes, using a current-sensing resistor in the supply path)

(In the four battery-discharge profile graphs below, the blue traces show the battery terminal voltages; the red traces show the forward voltage of the LED cluster)

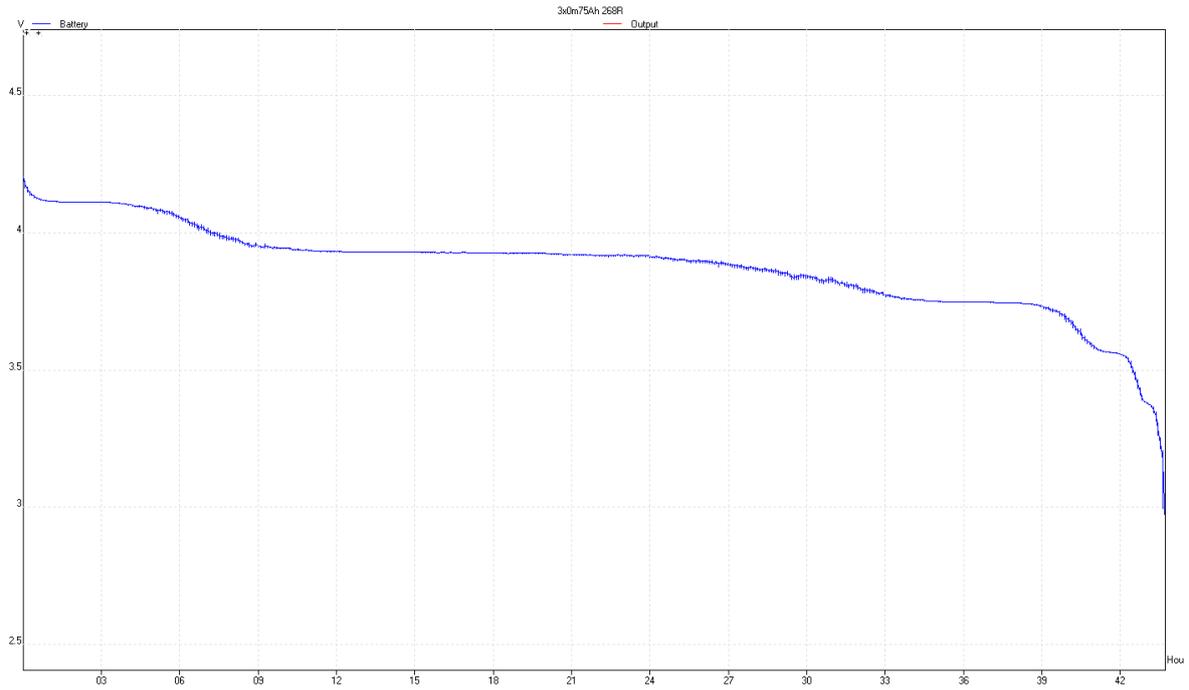


Fig 3 - Battery Discharge profile, 268R

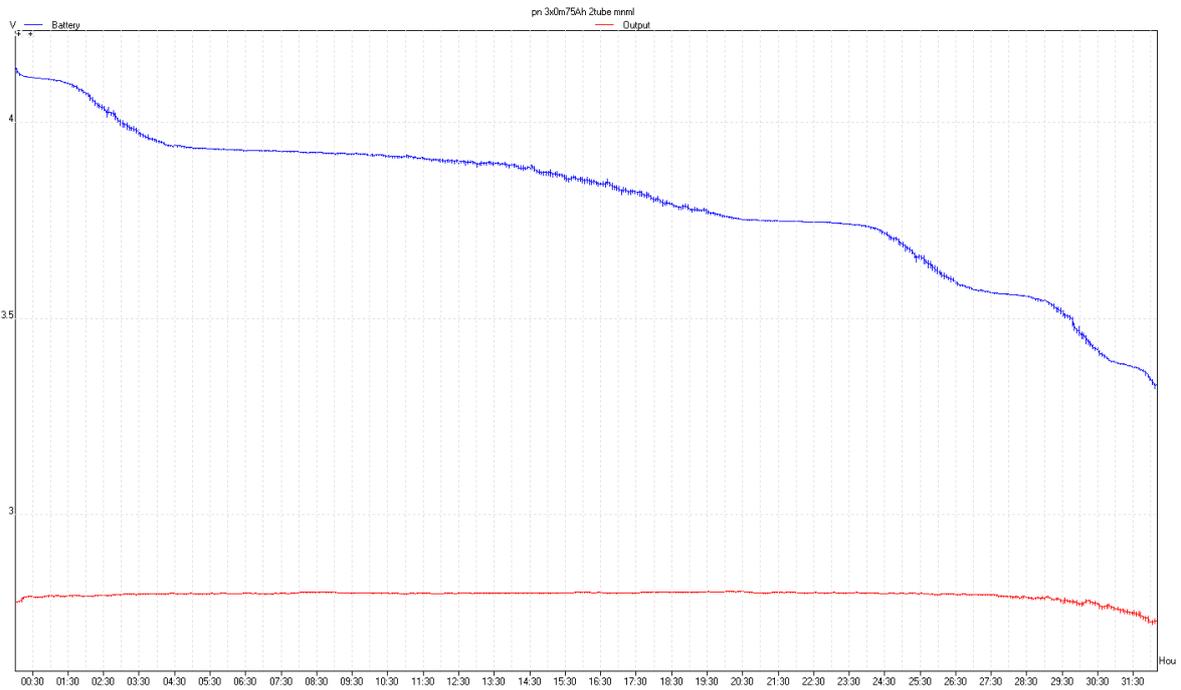


Fig 4 - Battery Discharge profile, 'no-feedback' circuit

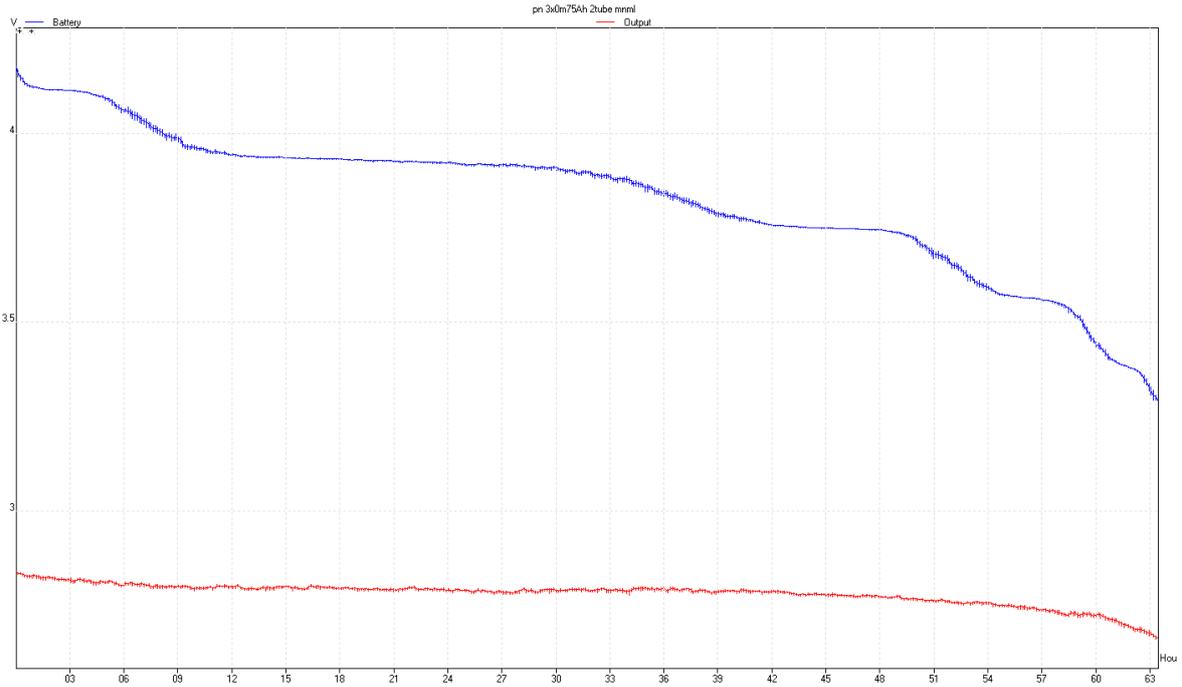


Fig 5 - Battery Discharge profile, 'with-feedback' circuit

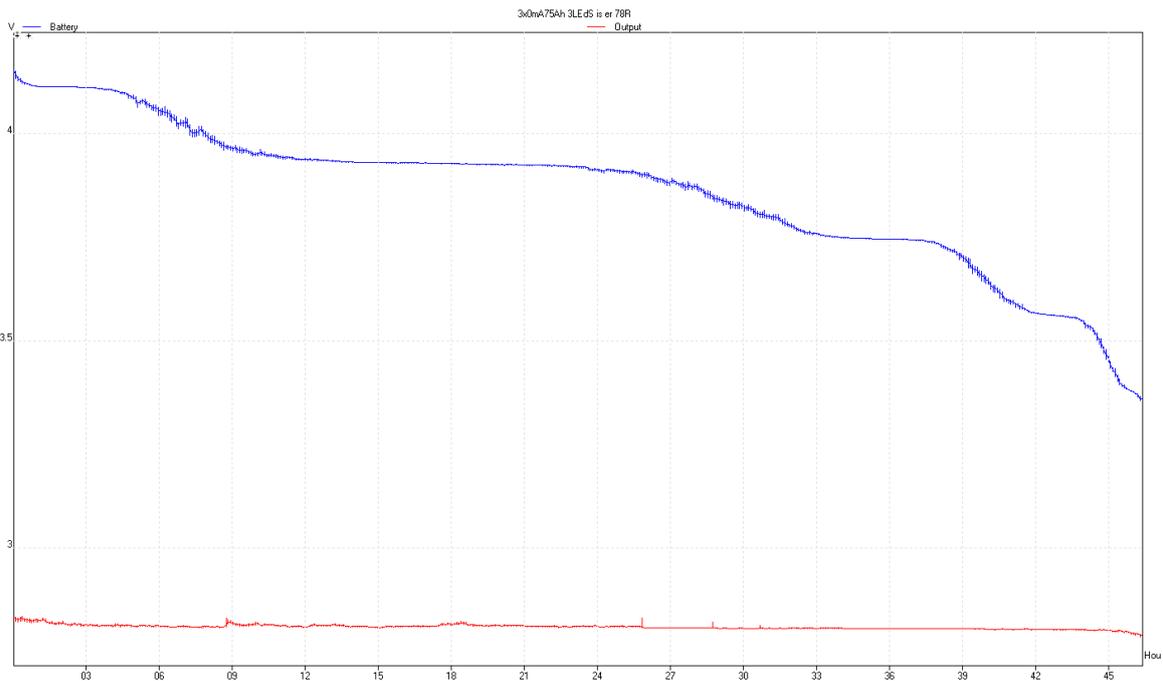


Fig 6 - Battery Discharge profile, LED cluster, 78R (in series)

As a comparison, an additional battery-discharge profile was logged using a load comprising a 78R (measured) resistor in series with the same LED cluster as used in the test circuits

The series resistance was chosen to produce an average current-draw similar to that of the series 268R resistance load, which gives a value between those of the 'With-Feedback' and 'No-Feedback' configurations of the test circuit

In the battery-discharge profile shown in Fig. 6 the mid-duration LED output was measured as approx. 140 foot-candles at 6"